

$$V_1^e = V_0 \frac{Z_{in}^e}{Z_{in}^e + Z_0}, \quad V_1^o = V_0 \frac{Z_{in}^o}{Z_{in}^o + Z_0}$$

$$Z_{in}^e = Z_{0e} \frac{\sqrt{Z_{0o}} + j\sqrt{Z_{0e}} \tan \theta}{\sqrt{Z_{0e}} + j\sqrt{Z_{0o}} \tan \theta}, \quad Z_{in}^o = Z_{0o} \frac{\sqrt{Z_{0e}} + j\sqrt{Z_{0o}} \tan \theta}{\sqrt{Z_{0o}} + j\sqrt{Z_{0e}} \tan \theta}$$

$$\frac{Z_{in}^e}{Z_{in}^e + Z_0} = \frac{Z_{0e} (\sqrt{Z_{0o}} + j\sqrt{Z_{0e}} \tan \theta)}{Z_{0e} (\sqrt{Z_{0o}} + j\sqrt{Z_{0e}} \tan \theta) + \sqrt{Z_{0e} Z_{0o}} (\sqrt{Z_{0e}} + j\sqrt{Z_{0o}} \tan \theta)} = \frac{Z_{0e} (\sqrt{Z_{0o}} + j\sqrt{Z_{0e}} \tan \theta)}{2Z_{0e} \sqrt{Z_{0o}} + j\sqrt{Z_{0e}} (Z_{0e} + Z_{0o}) \tan \theta}$$

$$\frac{Z_{in}^e}{Z_{in}^e + Z_0} = \frac{Z_0 + jZ_{0e} \tan \theta}{2Z_0 + j(Z_{0e} + Z_{0o}) \tan \theta}$$

$$\frac{Z_{in}^o}{Z_{in}^o + Z_0} = \frac{Z_0 + jZ_{0o} \tan \theta}{2Z_0 + j(Z_{0e} + Z_{0o}) \tan \theta}$$


$$V_3 = V_3^e + V_3^o = V_1^e - V_1^o = V_0 \frac{j(Z_{0e} - Z_{0o}) \tan \theta}{2Z_0 + j(Z_{0e} + Z_{0o}) \tan \theta}$$

Defining

$$C = \frac{Z_{0e} - Z_{0o}}{Z_{0e} + Z_{0o}}, \quad \sqrt{1 - C^2} = \frac{2Z_0}{Z_{0e} + Z_{0o}}$$

$$V_3 = V_0 \frac{jC \tan \theta}{\sqrt{1 - C^2} + j \tan \theta}$$

V_2 and V_4

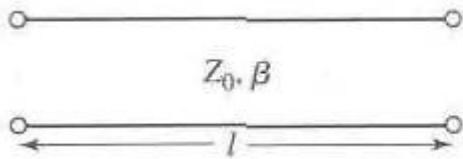

$$A = \cos \beta l$$

$$B = jZ_0 \sin \beta l$$

$$C = jY_0 \sin \beta l$$

$$D = \cos \beta l$$

$$\begin{bmatrix} V_1^{eo} \\ I_1^{eo} \end{bmatrix} = \begin{bmatrix} \cos \theta & jZ_{0eo} \sin \theta \\ jY_{0eo} \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} V_2^{eo} \\ -I_2^{eo} \end{bmatrix} \implies \begin{bmatrix} V_2^{eo} \\ -I_2^{eo} \end{bmatrix} = \begin{bmatrix} \cos \theta & -jZ_{0eo} \sin \theta \\ -jY_{0eo} \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} V_1^{eo} \\ I_1^{eo} \end{bmatrix}$$

$$V_2^e = V_1^e \cos \theta - jZ_{0eo} I_1^{eo} \sin \theta$$

$$V_1^e = V_0 \frac{Z_{in}^e}{Z_{in}^e + Z_0} = V_0 \frac{Z_0 + jZ_{0e} \tan \theta}{2Z_0 + j(Z_{0e} + Z_{0o}) \tan \theta}$$

$$I_1^e = \frac{V_0}{Z_{in}^e + Z_0} = \frac{V_0 (\sqrt{Z_{0e}} + j\sqrt{Z_{0o}} \tan \theta)}{2Z_{0e}\sqrt{Z_{0o}} + j\sqrt{Z_{0e}}(Z_{0e} + Z_{0o}) \tan \theta} = \frac{V_0 (Z_0 + jZ_{0o} \tan \theta)}{2Z_0^2 + jZ_0 (Z_{0e} + Z_{0o}) \tan \theta}$$

$$V_2^e = V_0 \frac{(Z_0 + jZ_{0e} \tan \theta) \cos \theta - jZ_{0e} (1 + jZ_{0o} \tan \theta / Z_0) \sin \theta}{2Z_0 + j(Z_{0e} + Z_{0o}) \tan \theta} = V_0 \frac{Z_0}{2Z_0 \cos \theta + j(Z_{0e} + Z_{0o}) \sin \theta}$$

$$V_2^o = V_0 \frac{Z_0}{2Z_0 \cos \theta + j(Z_{0e} + Z_{0o}) \sin \theta}$$

$$V_2 = V_2^e + V_2^o = V_0 \frac{2Z_0}{2Z_0 \cos \theta + j(Z_{0e} + Z_{0o}) \sin \theta} = V_0 \frac{\sqrt{1-C^2}}{\sqrt{1-C^2} \cos \theta + j \sin \theta}$$

$$V_3 = V_2^e - V_2^o = 0$$

$$a_1 = \frac{V_1 + I_1 Z_0}{2\sqrt{Z_0}} = \frac{V_0}{\sqrt{Z_0}}, \quad b_1 = 0$$

$$b_2 = \frac{V_2 - I_2 Z_0}{2\sqrt{Z_0}} = \frac{V_2}{\sqrt{Z_0}} = \frac{V_0}{\sqrt{Z_0}} \frac{\sqrt{1-C^2}}{\sqrt{1-C^2} \cos \theta + j \sin \theta}$$

$$b_3 = \frac{V_3}{\sqrt{Z_0}} = \frac{V_0}{\sqrt{Z_0}} \frac{jC \tan \theta}{\sqrt{1-C^2} + j \tan \theta}$$

$$b_4 = 0$$