# Sheet 4

# Question (1)

Consider a two-port network consisting of a junction of two transmission lines with characteristics impedances  $Z_{01}$  and  $Z_{02}$ , as shown in the below. Find the generalized scattering parameters of this network.



#### Question (2)

Use the ABCD matrices to find the voltage  $V_L$  across the load resistor in the circuit shown below.



#### Question (3)

The four-port 90° hybrid coupler has the following scattering matrix,



If ports 2 and 3 are terminated with equal adjustable loads  $Z_L$  as shown in the figure.

- (a) Find the scattering matrix for the resulting two-port network (between port 1 and 4).
- (b) Show that the resulting 2-port network represents an attenuator, and plot the attenuation as a function of  $Z_L/Z_0$ , for  $0 \le Z_L/Z_0 \le 10$  (Let  $Z_L$  be real).

Faculty of Engineering Cairo University Electronics and Electrical Engineering Dept.

# Question (4)

Consider the T-junction of three lines with characteristic impedances  $Z_1$ ,  $Z_2$ , and  $Z_3$ , as shown below. Demonstrate the it is impossible for all three lines to be matched, when looking toward the junction.



# Question (5)

Two identical 90° coupler with C=8.34 dB are connected as shown below. Find the resulting phase and amplitudes at ports 2' and 3', relative to port 1.



Question (6)

Consider the T and  $\Pi$  resistive attenuator circuits shown below. If the input and the output are matched to  $Z_0$ , and the ratio of output voltage to input voltage is  $\alpha$ , derive the design equations for  $R_1$  and  $R_2$  for each circuit. If  $Z_0 = 50 \Omega$ , compute  $R_1$  and  $R_2$  for 3 dB, 10 dB, and 20 dB attenuators of each type.



Question (7)

Design a three-port resistive divider for an equal power split and a 100  $\Omega$  system impedance. If port 3 is matched, calculate the change in the output power at port 3 (in dB) when port 2 is connected first to a matched load, and then to a load having mismatch of  $\Gamma = 0.3$ .



Faculty of Engineering Cairo University Electronics and Electrical Engineering Dept.

### Question (8)

Consider the general branch-line coupler shown below, having shunt arm characteristic impedances  $Z_a$ , and series arm impedance  $Z_b$ . Using an even-odd mode analysis, derive design equations for a quadrature hybrid coupler with arbitrary power division ration  $\alpha = P_2/P_3$ , and with the input port (port 1) matched. Assume all arms are  $\lambda/4$  long. Is port 4 isolated in general.

