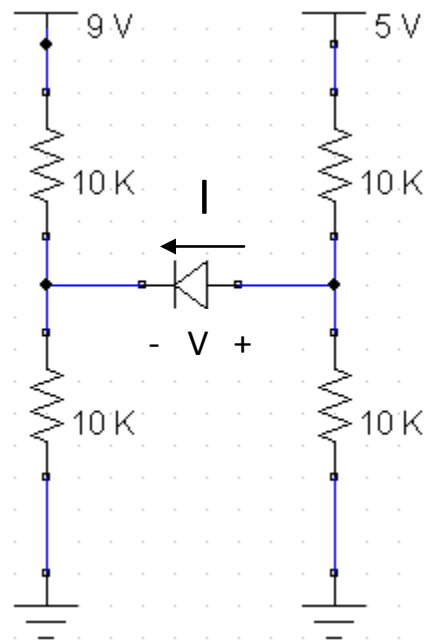


1) Same as problem 5

Assuming ideal Diodes, find the labeled current and voltages



2) The circuit shown is a model of a battery charger. Here  $V_1$  is a 10-V peak sine wave,  $D_1$  and  $D_2$  are ideal diodes,  $I$  is a 100mA current source, and  $B$  is a 4.5-V battery.

Sketch the waveform of the battery current  $I_B$ . What is its peak value? What is its average value?

If the peak value of  $V_1$  is reduced by 10%, what do the peak and average values of  $I_B$  become?

