

## Sheet 1: Revision

1)

a) For the current source shown in fig (1-a), derive an approximate expression for  $I_{o1}$  and  $I_{o2}$  as functions of  $V_{cc}$ . [Assume matched transistors]

b) If the current source of fig (p1-a) is replaced by the current source of fig (p1-b), find the new values of  $I_{o1}$ ,  $I_{o2}$  as functions of  $V_{cc}$  [Assume matched transistors]

c) Which of the two circuits do you prefer from the point of view of IC fabrication?

d) For the source shown in fig(p1-c), find the relation between  $I_{out2}$ ,  $I_{out3}$ , and  $I_{ref}$  [ $W/L_{M3}=2W/L_{M1,M2}$ ]

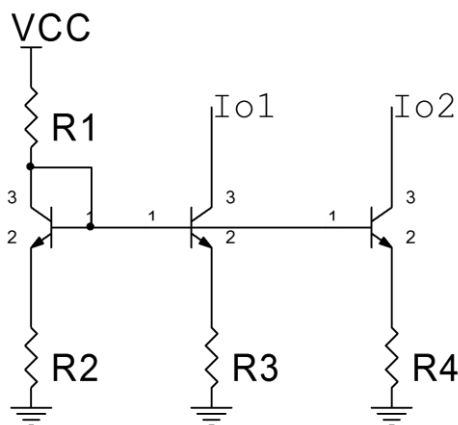


Fig (p1-a)

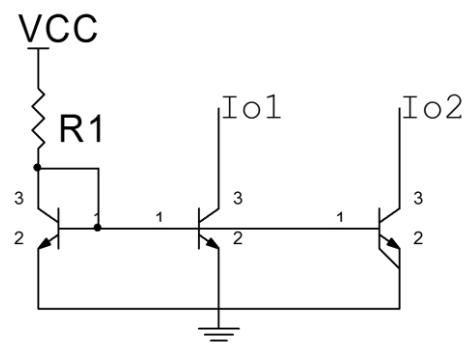


Fig (p1-b)

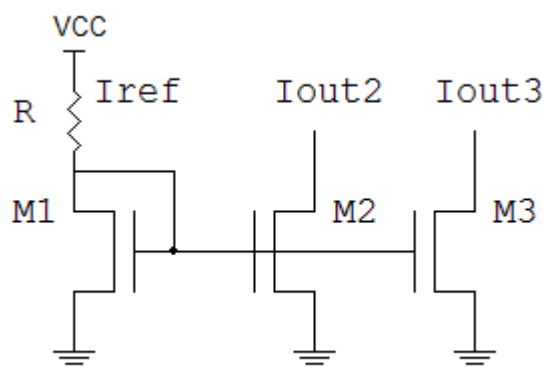


Fig (p1-c)

- 2) For the following circuit, draw the output in time domain and determine the maximum value of the signal, the input is a square wave signal alternating from 0 and 5V, draw the output for two cases:  
 a- Input frequency is 100 Hz.  
 b- Input frequency is 1 KHz.

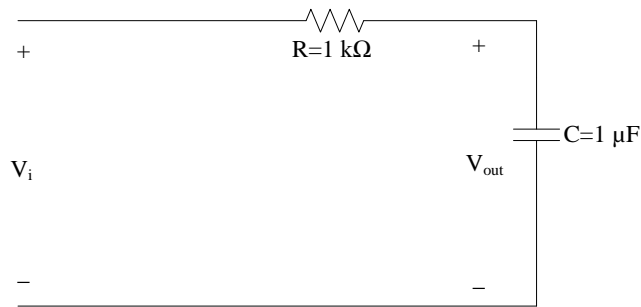


Fig (p2)

- 3) The following diode network is used to change the circuit output level from 15,-15 to 5,-5. For each circuit design the zener diode. If the maximum current that the opamp can supply is 5 mA, what is the minimum R value can be used?

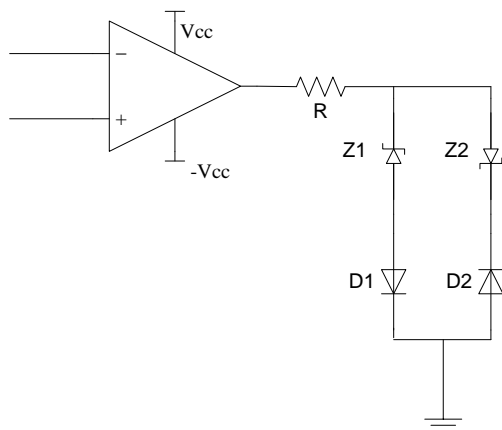


Fig (p3-a)

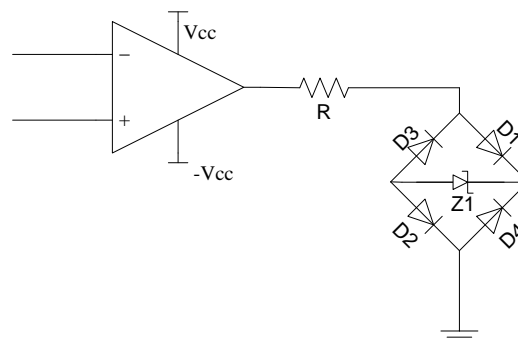


Fig (P3-b)

4) Draw the layout for the following circuits, state which circuit is better.

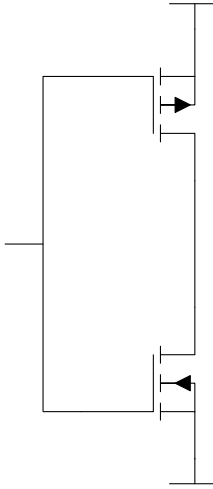


Fig (p4-a)

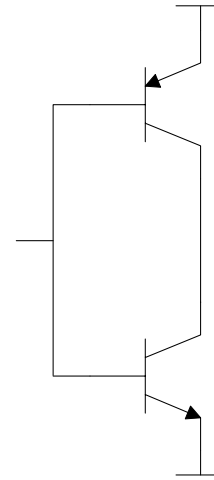


Fig (p4-b)