

Sheet 2: Linear Op-Amp Circuit Applications

1. An almost ideal op-amp has an open-circuit output voltage $V_o = 10V$ and a gain $A=100dB$.
 - a) What is the input voltage V_{id} ?
 - b) How large gain must be to make $V_{id} \leq 1\mu V$?
2. Assuming ideal op-amp, find the gain and input resistance for the following circuits:

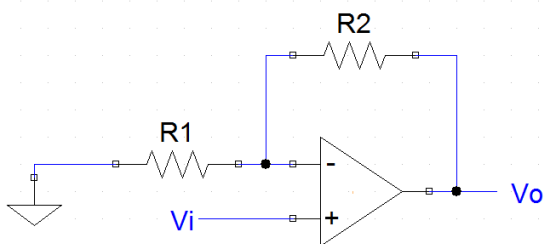


Fig. (P2-a)

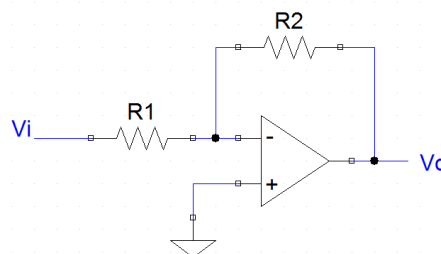


Fig.(P2-b)

3. Assuming ideal op-amp, write V_o as a function of V_1 & V_2 in the following figure. Can you suggest an application for this circuit?

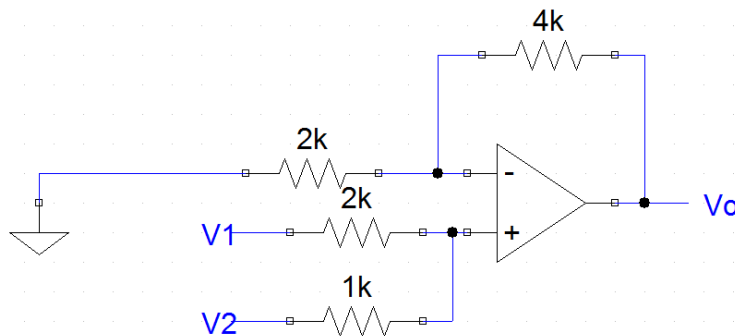


Fig. (P3)

4.
 - a) Assuming ideal Op-amp, what are the gain, input resistance, and output resistance of the amplifier in Fig.(P4) if $R_1= 180 \Omega$ and $R_2 = 47 k\Omega$? Express the gain in dB.
 - b) If the resistors have 10% tolerances, what are the worst-case values (highest and lowest) of gain that could occur? What are the resulting positive and negative tolerances on the voltage gain with respect to the ideal value?

- c) Show the contradiction in satisfying both the gain and input resistance conditions for a typical inverting voltage amplifier and how this problem can be alleviated with a non-inverting configuration

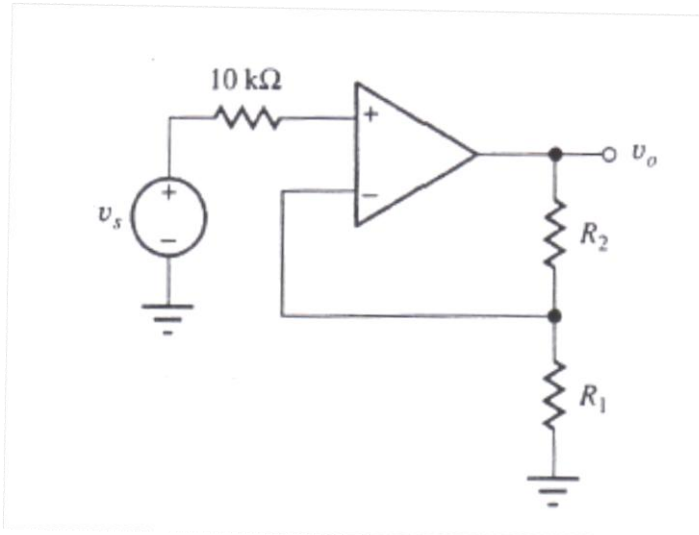


Fig. (P4)

5. For the following circuit:

- Get V_O in terms of V_{I1} & V_{I2} .
- Find the condition on the resistances to use it as a difference amplifier. Then calculate the common mode gain, differential input resistance and the CMRR. State the main disadvantage to use it as a difference amplifier.

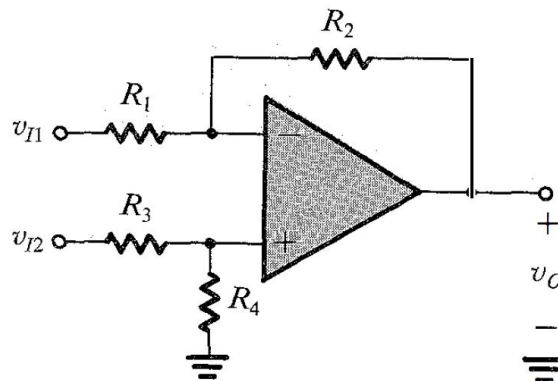


Fig. (P5)

6. What is the voltage gain of the instrumentation amplifier in Fig. (P6) if $R_1=20\text{ k}\Omega$, $R_2=100\text{ k}\Omega$, $R_3=10\text{ k}\Omega$ and $R_4=10\text{ k}\Omega$. Write an expression for the output voltage if

$v_1 = 4 - 0.1\sin(4000\pi t)$ V and $v_2 = 4 + 0.1\sin(4000\pi t)$ V. Discuss its advantages over a regular difference amplifier.

7.

- The input voltage of the integrator circuit in Fig. (P7) is a rectangular pulse with amplitude of 5 V and a width 1ms. Draw the waveform at the output of the integrator if the pulse starts at $t=0$, $R=10$ k Ω and $C=0.1$ μ F. Assume $v_0 = 0$ for $t \leq 0$.
- Repeat (a) if the capacitor is initially charged to 0.5 V, i.e. $v_0 = 0.5$ V for $t \leq 0$. Suggest a method to eliminate this initial voltage.

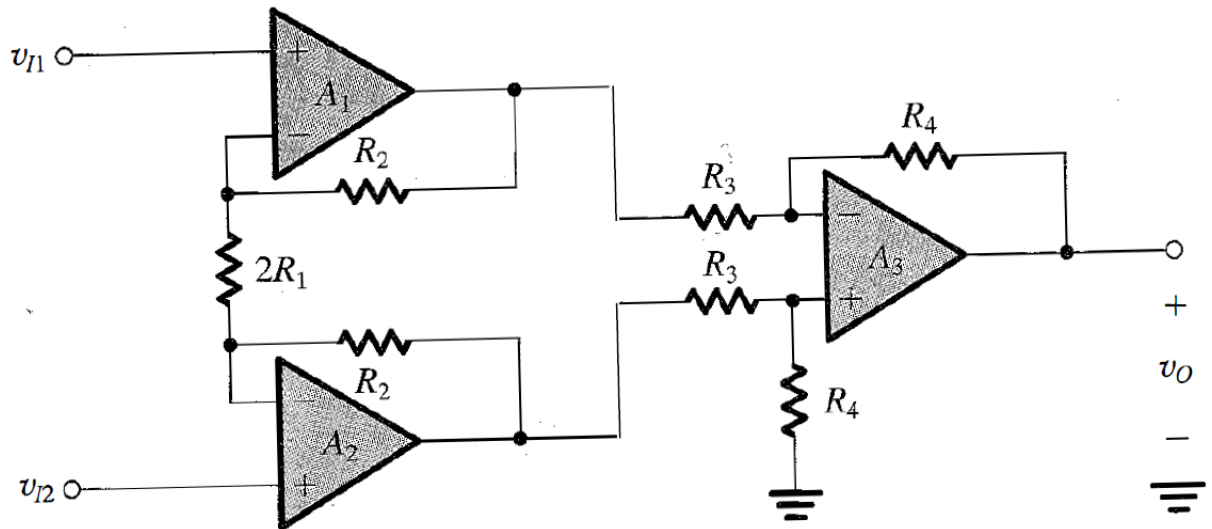


Fig. (P6)

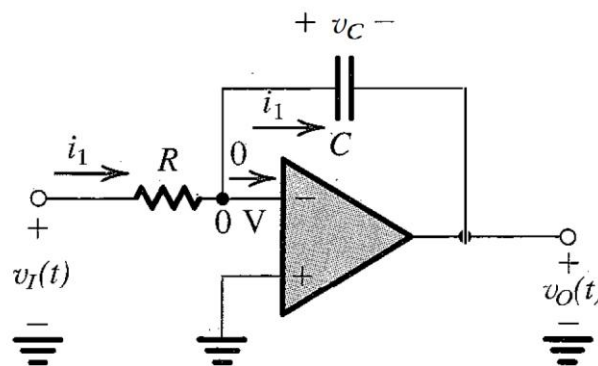


Fig. (P7)

- Assuming ideal op-amp, find the relation between V_i and V_o for the following circuit. State its function.

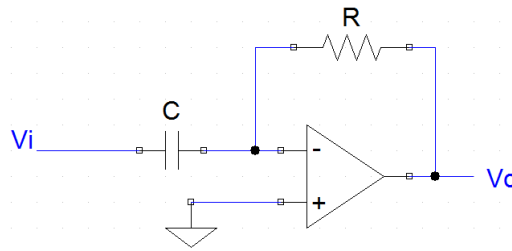


Fig. (P8)

9. Show, using ideal Op-Amps, how to realize a PID controller that has the input/output relation: $y = k_1x + k_2 \int x dt + k_3 \frac{dx}{dt}$. Find the constants k_1 , k_2 and k_3 in terms of the used resistors and/or capacitors.

Op-Amps non-idealities:

10. Find the gain and input resistance for the circuits in Fig. (P10) if the Op-amp has finite open loop gain (A) and input resistance (R_{in})

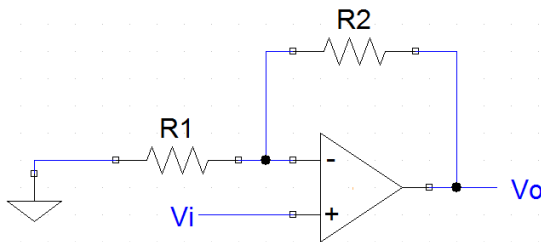


Fig. (P10-a)

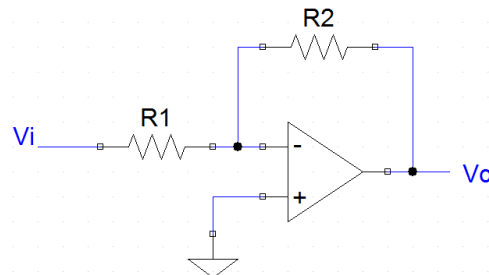


Fig. (P10-b)

11. Calculate the worst-case output voltage for the circuit in Fig. (P11) if $V_{OS} = 1\text{mV}$, $I_{B1} = 100\text{ nA}$, and $I_{B2} = 95\text{ nA}$. What would the ideal output voltage be? What is the total error in this circuit? Is there a better choice for the value of R_1 ? If so, what is the value?

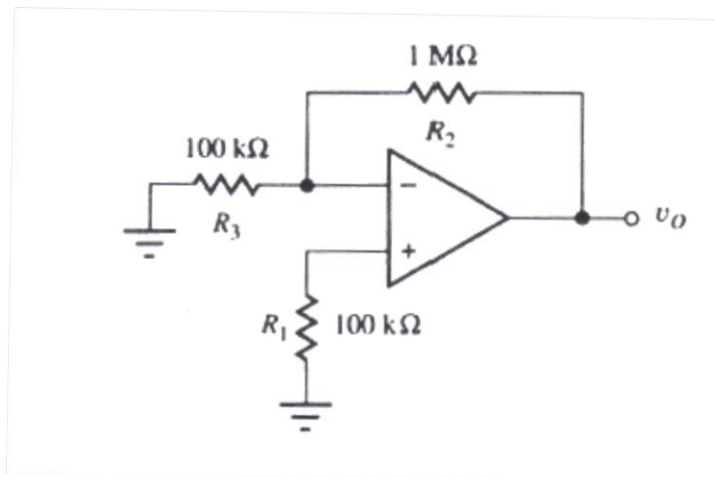


Fig. (P11)