

Sheet 3

Continue: Practical considerations on Op-Amp

- 1) Assuming the slew-rate of the op-amp is due to charging the compensation capacitor with a constant current. Determine the value of this current for the op-amp to be capable of changing its output from $-V_{CC}$ to V_{CC} in a time of at least $10\mu\text{sec}$.
- 2) Find the gain and output resistance of a non-inverting amplifier with $R_1= 1\text{ k}\Omega$ and $R_2= 39\text{ k}\Omega$, assuming non-ideal Op Amp with $A= 80\text{ dB}$ and $R_o= 50\ \Omega$.
- 3) For the shown Op Amp in figure (p3), $A= 80\text{ dB}$ and $\text{CMRR}= 60\text{ dB}$. Calculate the gain error.

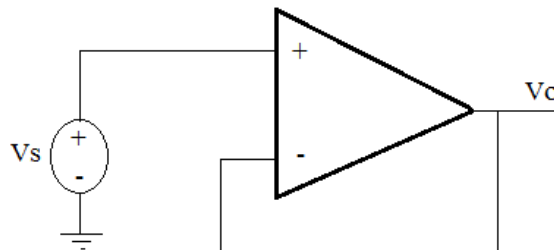


Fig (p3)

- 4) In figure (p4) assume ideal Op Amp, the resistance nominal value is $R= 10\text{ k}\Omega$ with 5% tolerance. Find the worst case value of CMRR in dB.

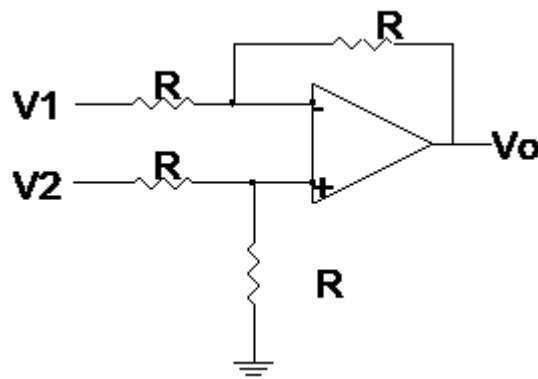


Fig (p4)