

Sheet 6 MOS Logic Gates

Problem 1)

For the inverters below, find:

V_{OH} , V_{OL} , V_{IH} and V_{IL} In terms of transistors parameters.

Hint: Take $V_{Tn} = |V_{Tp}|$

 


Figure (1)

 


Figure (2)

Problem 2)

- a) Implement the logic function ($F' = ABC + DE'$) using static CMOS. Assume inverted inputs are available.
- b) Size the transistors so that ($t_{pLH} = t_{pHL}$) in the worst case, and both are half the unit inverter delay.
- c) Find approximate area of the gate designed if the technology used is 90nm.
- d) Find the best case t_{pLH} and t_{pHL} .

Problem 3)

If $C_L = 1$ pF, and each internal node has 0.1 pF capacitor. Over two cycles:

- What is the logic function of this gate?
- What is the input pattern that causes worst charge sharing?
- Find the value of the output voltage in this case.

